

Problem 9.1:

a-) The numbers we should represent are from 0 to 6. Hence, we will need three inputs to represent it in binary.

Let's take x_0, x_1, x_2 such as x_0, x_1 and x_2 Base 2 representation.

⇒ Base 7 numerals can be converted to binary using three binary digits and the following table.

x_0	x_1	x_2	base 7
0	0	0	0
0	0	1	1
0	1	0	2
0	1	1	3
1	0	0	4
1	0	1	5
1	1	0	6

⇒ We will then use three input lines x_0, x_1, x_2 representing the three binary digits to generate 7 binary patterns representing the base 7 digits from 0 to 6.

	0	*	0	*	*	*	*
	000	000	000	000	000	000	000
base 7	0	1	2	3	4	5	6
Binary	000	001	010	011	100	101	110

⇒ We will then use logic gates circuits to control each of the 6 LED based on the three inputs x_0, x_1, x_2 .

⇒ We will need 7 outputs one for each LED. So let's investigate each LED one at a time.

* From the previous table we can deduct the following:

LED A is ON : 001; 011; 100; 101; 110
OFF : 000; 010

LED B, C is ON : 010; 011; 100; 101; 110
OFF : 000; 001

LED D, F is ON : 101; 110
OFF : 000; 001; 010; 011; 100

LED E is ON : 100; 110
OFF : 000; 001; 010; 011; 101

Truth tables:

LED A:

Input			Output
x_0	x_1	x_2	LED A
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1

LED B and C:

Input			Output
x_0	x_1	x_2	LED B and C
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1

LED D and F:

Input			Output
x_0	x_1	x_2	LED D and F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1

LED E:

Input			Output
x_0	x_1	x_2	LED E
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1

b-) The previous truth tables can be each converted to a K-map which will help us define the boolean expressions.

Karnaugh Map:

LED A:

$x_0 \backslash x_1$	00	01	10	11
x_2	0	0	0	1
	1	1	1	1

$$\Rightarrow x_0 + x_2$$

LED B and C:

$x_0 \backslash x_1$	00	01	10	11
x_2	0	0	1	1
	1	0	1	1

$$\Rightarrow x_0 + x_1$$

LED D and F:

$x_0 \backslash x_1$	00	01	10	11
x_2	0	0	0	1
	1	0	0	1

$$\Rightarrow x_0 x_1 + x_0 x_2$$

LED E:

$x_0 \backslash x_1$	00	01	10	11
x_2	0	0	0	1
	1	0	0	0

$$\Rightarrow x_0 x_2$$